

IT@CookBook, 처음 만나는 회로이론(2판)

[연습문제 답안 이용 안내]

- 본 연습문제 답안의 저작권은 방성완과 한빛아카데미(주)에 있습니다.
- 이 자료를 무단으로 전제하거나 배포할 경우 저작권법 136조에 의거하여 최고 5년 이하의 징역 또는 5천만원 이하의 벌금에 처할 수 있고 이를 병과(併科)할 수도 있습니다.

Chapter 01 연습문제 해답

1.1 -1.602×10^{-13} [C]

1.2 $6e^{-2t}$ [A], $-3(e^{-2} - 1)$ [C]

1.3 $G = 1$ [mS], $R = 1$ [k Ω]

1.4 20 [V]

1.5 10 [mV]

1.6 (a) 10 [W] (b) -6 [W]

1.7 전압원 V_A : 50 [W] (소모)
전압원 V_B : 100 [W] (소모)
전압원 V_C : -150 [W] (공급)

1.8 $i = 7$ [A]

1.9

- (1) 접점 1: $i_6 = -i_1 = -2$ [A]
- (2) 접점 3: $i_2 = i_3 = 3$ [A]
- (3) 접점 5: $i_4 = -i_5 = -4$ [A]
- (4) 접점 2: $i_8 = -i_1 - i_2 + i_7 = -2 - 3 + 1 = -4$ [A]
- (5) 접점 4: $i_9 = -i_3 - i_4 - i_8 = -3 - (-4) - (-4) = 5$ [A]

1.10

- (1) 루프 I: $v_2 = v_1 + v_3 = 1 + 2 = 3$ [V]
- (2) 루프 III: $v_5 = -v_3 + v_6 = -2 + 3 = 1$ [V]
- (3) 루프 IV: $v_7 = -v_6 + v_9 = -3 + 5 = 2$ [V]
- (4) 루프 II: $v_4 = v_5 - v_8 = 1 - 4 = -3$ [V]

1.11 접점: 6개, 분기: 8개

1.12 $i = 1$ [A]

1.13 $v_1 = 2 \times (-3) = -6$ [V], $v_2 = -3 \times (-3) = 9$ [V]

1.14 $v_1 = 15$ [V], $v_2 = 25$ [V]

1.15 $6 + 4 = 10$ [Ω]

1.16 $G_{eq} = 10 \parallel 40 = \frac{10 \cdot 40}{10 + 40} = 8$ [S]

1.17 $i = 1$ [A]

1.18

- (a) $i = \frac{2}{10} \frac{[A \cdot h]}{[h]} = 0.2$ [A]
- (b) $P = VI = 9 \times 0.2 = 1.8$ [W]
- (c) $W = Pt = 1.8 \times 10 = 0.018$ [kWh]

1.19 $i_1 = \frac{30}{10} = 3$ [A], $i_2 = \frac{30}{6} = 5$ [A], $i_3 = \frac{30}{5} = 6$ [A]

1.20 첫 번째 띠: 갈색, 두 번째 띠: 파랑, 세 번째 띠: 빨강

Chapter 02 연습문제 해답

2.1 $R_2 = 500 \text{ } [\Omega]$

2.2 $v_3 = V_s \times \frac{8}{R_{eq}} = 3 \times \frac{8}{24} = 1 \text{ [V]}$

2.3 $v_1 = 12 \times \frac{2}{2+4} = 4 \text{ [V]}, \quad v_2 = 12 \times \frac{4}{2+4} = 8 \text{ [V]}$

2.4 $i_1 = 20 \times \frac{4}{6+4} = 8 \text{ [mA]}$

$$i_2 = 12 \times \frac{5}{20+5} = 2.4 \text{ [mA]}$$

$$i_3 = 12 \times \frac{20}{20+5} = 9.6 \text{ [mA]}$$

2.5 $i_1 = \frac{20}{R_{eq}} = 4 \text{ [A]}$

$$i_2 = i_1 \times \frac{R_{eq1}}{R_{eq1} + 12} = 4 \times \frac{4}{4+12} = 1 \text{ [A]}$$

$$i_3 = i_1 \times \frac{12}{R_{eq1} + 12} = 4 \times \frac{12}{4+12} = 3 \text{ [A]}$$

$$i_4 = i_3 \times \frac{5}{20+5} = 0.6 \text{ [A]}$$

$$i_5 = i_3 \times \frac{20}{20+5} = 2.4 \text{ [A]}$$

2.6 $i_1 = 2v_1 = -\frac{2}{3} \text{ [A]}, \quad i_2 = 3v_2 = -\frac{1}{3} \text{ [A]}$

$$2.7 \quad v_A = \frac{12}{5} [\text{V}], \quad v_B = -\frac{4}{5} [\text{V}]$$

$$2.8 \quad I_2 = \frac{3}{2}(-4) = -6 [\text{A}]$$

$$2.9 \quad 9 [\text{A}]$$

$$2.10 \quad I_1 = 5 [\text{A}], \quad I_2 = -1 [\text{A}]$$

$$2.11 \quad 12 [\text{V}]$$

$$2.12 \quad 10 [\text{V}]$$

$$2.13 \quad -1.2 [\text{A}]$$

$$2.14 \quad -6 [\text{V}]$$

$$2.15 \quad P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{4^2}{4 \times 3} = \frac{4}{3} [\text{W}]$$

$$2.16 \quad R_{Th} = (20 + 30) \parallel (40 + 10) = \frac{50 \times 50}{50 + 50} = 25 [\Omega]$$
$$V_{Th} = 30 \times 3 - 20 \times 2 = 50 [\text{V}]$$

$$2.17 \quad i_{out} = 0 \text{ [A]}, \quad R_N = \frac{v_{out}}{i_{out}} = \frac{1}{0} = \infty \quad (\text{기방회로})$$

$$2.18 \quad R_N = (20 + 30) \parallel (40 + 10) = \frac{50 \times 50}{50 + 50} = 25 \text{ [\Omega]}$$

$$I_N = \frac{V_N}{R_N} = \frac{50}{25} = 2 \text{ [A]}$$

$$2.19 \quad R_N = (15 + 25) \parallel 10 = \frac{40 \times 10}{40 + 10} = 8 \text{ [\Omega]}, \quad I_N = 6 \text{ [A]}$$

$$2.20 \quad P_L = \frac{V_L^2}{R_L} = \frac{8^2}{10} = 6.4 \text{ [W]}, \quad 50\%$$

Chapter 03 연습문제 해답

3.1 $i_C(t) = C \frac{dv_C(t)}{dt} = (60 \times 10^{-3}) \frac{220 - 120}{6} = 1 \text{ [A]}$

3.2 $W_C = 100 \text{ [\mu J]}$

3.3 $P_C(t) = v_c(t)i_C(t) = e^{-2t} \times (-6 \times 10^{-6} e^{-2t}) = -6e^{-4t} \text{ [\mu W]}$

3.4 $v_1 = 10i_1 = 10 \text{ [V]}, \quad v_2 = 40 - 25i_1 = 15 \text{ [V]}$

3.5 $C_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{15} + \frac{1}{20} + \frac{1}{30}} = 4 \text{ [mF]}$

3.6 $C = 10 \text{ [\mu F]}$

3.7 $C_{eq} = 4 + 6 = 10 \text{ [F]}$

3.8 $C_{eq} = C_{eq1} + C_{eq2} = 5 + 5 = 10 \text{ [mF]}$

3.9 $C_{eq} = \frac{2 \times 2}{2 + 2} = 1 \text{ [F]}$

3.10 $v_4 = v_2 - v_3 = 45 - 30 = 15 \text{ [V]}$

$$3.11 \quad v_L(t) = L \frac{di_L(t)}{dt} = (6 \times 10^{-3}) \frac{(100 - 50) \times 10^{-3}}{2 \times 10^{-3}} = 150 \text{ [mV]}$$

$$3.12 \quad W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 2 \times 10^{-3} \times (10)^2 = 0.1 \text{ [J]}$$

$$3.13 \quad P_L(t) = v_L(t)i_L(t) = -10 \times 10^{-3} e^{-t/2} \times (e^{-t/2}) = -10e^{-t} \text{ [mW]}$$

$$3.14 \quad i_L = \frac{2}{8+2} \times 10 = 2 \text{ [A]}, \quad W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 5 \times 10^{-3} \times 2^2 = 10 \text{ [mJ]}$$

$$3.15 \quad L_{eq} = 0.1 \text{ [H]}$$

$$3.16 \quad L_{eq} = \frac{1}{\frac{1}{12} + \frac{1}{10} + \frac{1}{20} + \frac{1}{60}} = 4 \text{ [mH]}$$

3.17 첫 번째 띠: 노랑, 두 번째 띠: 검정, 세 번째 띠: 빨강, 네 번째 띠: 금색

$$3.18 \quad L_{eq} = \frac{50 \times 50}{50 + 50} = 25 \text{ [mH]}$$

$$3.19 \quad L_{eq} = \frac{20 \times 5}{20 + 5} = 4 \text{ [H]}$$

$$3.20 \quad L = 40 \text{ [mH]}$$

Chapter 04 연습문제 해답

4.1 $i_1 = 1, i_2 = -1, i_3 = -3$

4.2

$$\mathbf{A} = \begin{bmatrix} 2 & 4 & -1 & -3 \\ 1 & -3 & 7 & -2 \\ -3 & -2 & 6 & 1 \\ -1 & 1 & 4 & -3 \end{bmatrix}, \quad \mathbf{x} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}, \quad \mathbf{c} = \begin{bmatrix} -2 \\ 4 \\ 1 \\ 7 \end{bmatrix}$$

4.3

$$\left[\begin{array}{cccc|c} 2 & 4 & -1 & -3 & i_1 \\ 1 & -3 & 7 & -2 & i_2 \\ -3 & -2 & 6 & 1 & i_3 \\ -1 & 1 & 4 & -3 & i_4 \end{array} \right] = \begin{bmatrix} -2 \\ 4 \\ 1 \\ 7 \end{bmatrix}$$

4.4 $\mathbf{A}^{-1} = \frac{1}{2} \begin{bmatrix} 4 & -6 \\ -5 & 8 \end{bmatrix} = \begin{bmatrix} 2 & -3 \\ -5/2 & 4 \end{bmatrix}$

4.5 $\mathbf{A}^{-1} = \frac{1}{3} \begin{bmatrix} 5 & 2 & -1 \\ -2 & 1 & 1 \\ -2 & -2 & 1 \end{bmatrix} = \begin{bmatrix} 1.6667 & 0.6667 & -0.3333 \\ -0.6667 & 0.3333 & 0.3333 \\ -0.6667 & -0.6667 & 0.3333 \end{bmatrix}$

4.6 역행렬을 구할 수 없다.

$$4.7 \quad i_1 = \frac{\det(\mathbf{A}_1)}{\det(\mathbf{A})} = \frac{5}{5} = 1, \quad i_2 = \frac{\det(\mathbf{A}_2)}{\det(\mathbf{A})} = \frac{10}{5} = 2$$

$$4.8 \quad v_1 = \frac{|D_1|}{|D|} = \frac{0}{10} = 0, \quad v_2 = \frac{|D_2|}{|D|} = \frac{0}{10} = 0, \quad v_3 = \frac{|D_3|}{|D|} = \frac{10}{10} = 1$$

$$4.9 \quad v_C(t) = 7 - 5e^{-0.2t}$$

$$4.10 \quad i_L(t) = -e^{3t}$$

$$4.11 \quad v_C(t) = (1 + 2t)e^{-3t}$$

$$4.12 \quad i_L(t) = 2 - 8e^{-t} + 4e^{-2t}$$

$$4.13 \quad |z| = \sqrt{(-1)^2 + 1^2} = \sqrt{2}$$

$$4.14 \quad f(2 + j3) = 2(2 - j3) + j(2 + j3) + 3 = 4 - j4$$

$$4.15 \quad |2z - 3\bar{z}| = \sqrt{(-5)^2 + 10^2} = 5\sqrt{5}$$

$$4.16 \quad z = 1^{1/2} \left(\cos\left(-\frac{\pi}{2}\right) + i \sin\left(-\frac{\pi}{2}\right) \right)^{1/2} = \cos\left(-\frac{\pi}{4}\right) + i \sin\left(-\frac{\pi}{4}\right)$$

4.17 (a) $2\angle 120^\circ$ (b) 64

$$\mathbf{4.18} \quad e^z = e^{\ln 2 - i\pi} = e^{\ln 2} \cos(-\pi) + ie^{\ln 2} \sin(-\pi)$$

$$e^z = 2 \cos(\pi) = -2$$

$$\mathbf{4.19} \quad \left[\frac{1}{2} \left(\cos \frac{\pi}{12} + i \sin \frac{\pi}{12} \right) \right]^4 \left[2 \left(\cos \frac{\pi}{3} + i \sin \frac{\pi}{3} \right) \right]^5$$

$$= 2 \left[\cos \left(\frac{\pi}{3} + \frac{5\pi}{3} \right) + i \sin \left(\frac{\pi}{3} + \frac{5\pi}{3} \right) \right]$$

$$= 2(\cos 2\pi + i \sin 2\pi) = 2$$

$$\mathbf{4.20} \quad 3^{2-j} = 3^2 \cdot e^{\ln 3^{-j}} = 9e^{-j \ln 3} = 9[\cos(\ln 3) - j \sin(\ln 3)]$$

Chapter 05 연습문제 해답

5.1 $\tau = R_{eq}C = 150 \times 2 \times 10^{-3} = 0.3$ [sec]

5.2 $R = 5$ [kΩ], $C = 20$ [μF]

5.3 $v_C(t) = \frac{5}{10+5} \times 15 = 5$ [V]

5.4 $i(t) = -C \frac{dv_C(t)}{dt} = -\frac{1}{2} \left(-\frac{1}{5} \right) 12e^{-t/5} = 1.2e^{-0.2t}$ [A]

5.5 $\tau = 5$ [ms]

5.6 $R = \frac{v_L(t)}{i_L(t)} = \frac{200e^{-1000t}}{e^{-1000t}} = 200$ [Ω], $L = \frac{R}{1000} = \frac{200}{1000} = 0.2$ [H]

5.7 $i_L(t) = \frac{5}{10+5} \times 15 = 5$ [A]

5.8 $i(t) = i(0^-)e^{-t/\tau} = 1.54e^{-2t}$ [A]

5.9 $i(t) = \frac{20}{20+5} \times -i_L(t) = -8e^{-2t}$ [A]

5.10 과감쇠 응답 상태

$$5.11 \quad i_L(t) = (1+3t)e^{-3t} \text{ [A]}$$

$$5.12 \quad i_L(\infty) = 0 \text{ [A]}, \quad v_L(\infty) = 0 \text{ [V]}$$

$$5.13 \quad R = 2\sqrt{\frac{20 \times 10^{-3}}{8 \times 10^{-6}}} = 2 \times \frac{1}{2} \times 100 = 100 \text{ [\Omega]}$$

$$5.14 \quad v_C(t) = 3e^{-t} - 3e^{-3t} \text{ [V]}$$

$$5.15 \quad i(t) = \left(2\cos 3t + \frac{8}{3}\sin 3t \right) e^{-4t} \text{ [A]}$$

$$5.16 \quad i_L(t) = 20e^{-10t} - 5e^{-40t} \text{ [A]}$$

$$5.17 \quad v_C(t) = (8\cos t + 4\sin t)e^{-t/2} \text{ [V]} \\ i_C(t) = -2\sin te^{-t/2} \text{ [A]}$$

$$5.18 \quad v_{C_2}(t) = \left(\frac{RI_0C_2}{C_1 + C_2} + V_0 \right) e^{s_1 t} - \left(\frac{RI_0C_1}{C_1 + C_2} \right) e^{s_2 t} \text{ [V]}$$

$$5.19 \quad L = \frac{1}{C} = \frac{1}{100 \times 10^{-3}} = 10 \text{ [H]}$$

$$5.20 \quad i_L(t) = -30\sin\left(\frac{10}{3}t\right) \text{ [A]}$$

Chapter 06 연습문제 해답

6.1 (a) $-3\sin 2t = 3\cos(2t + 90^\circ)$

(b) $3\sin(2t - 40^\circ) = 3\cos(2t - 40^\circ - 90^\circ) = 3\cos(2t - 130^\circ)$

(c) $-3\sin(2t + 40^\circ) = 3\cos(2t + 40^\circ + 90^\circ) = 3\cos(2t + 130^\circ)$

6.2 진폭: $A = 2$, 위상: $\phi = -30^\circ$, 각주파수: $\omega = 2\pi$

고유 주파수: $f = \frac{\omega}{2\pi} = \frac{2\pi}{2\pi} = 1$ [Hz]

주기: $T = \frac{1}{f} = \frac{1}{1} = 1$ [s]

6.3 170° , 전류 $i_1(t)$ 가 전류 $i_2(t)$ 보다 170° 앞선 전류를 표시한다.

6.4 $V_{\text{rms}} = \sqrt{12} = 2\sqrt{3}$ [V]

6.5 $I_{\text{rms}} = \sqrt{40} = 2\sqrt{10}$ [A]

6.6 $f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) = 12 - \sum_{n=\text{홀 수}}^{\infty} \frac{16}{n\pi} \sin(nt)$

6.7 $\mathbf{I}(j\omega) = 10\angle 150^\circ$, $\mathbf{V}(j\omega) = 40\angle 150^\circ$

6.8 $v(t) = 10 \cos(3t - 120^\circ + 180^\circ) = -10 \cos(3t + 60^\circ)$ [V]

6.9 $v(t) = 5 \cos(10t - 36.87^\circ)$ [V]

6.10 (a) $i(t) = -2.93 \times \sqrt{2} \cos(20t + 45^\circ) = -4.14 \cos(20t + 45^\circ)$
 (b) (a)의 결과와 동일하게 된다.

6.11 $v(t) = 5 \cos(1000t - 30^\circ)$ [V]

6.12 $v(t) = 10 \cos(100t + 60^\circ)$ [V]

6.13 $Z_{eq}(j\omega) = 3 + 1 - j3 = 4 - j3$ [Ω]

6.14 $Z_{eq}(j\omega) = j30 + 10 + 30 - j10 = 40 + j20$ [Ω]

6.15 $Z_{eq} = \frac{1}{Y_{eq}} = \frac{25(4 - j3)}{(4 + j3)(4 - j3)} = 4 - j3$ [Ω]

6.16 $Y_{eq}(j\omega) = \frac{\frac{7}{3} \left(\frac{2}{3} + j \right) (3 - j)}{(3 + j)(3 - j)} = \frac{7}{10} + j \frac{49}{90}$ [S]

6.17 $i(t) = 0.5 \cos(10t + 45^\circ)$ [A]

6.18 $\mathbf{I}_o = \frac{-j2}{-j2 + 2} \mathbf{I}_2 = \frac{-j}{1-j} \cdot (-10 - j10) = \frac{-10(1-j)}{1-j} = -10$ [A]

6.19 $i_1(t) = 0.2 \cos(10t + 18.43^\circ)$ [A]

6.20 $C = 25$ [mF]

Chapter 07 연습문제 해답

7.1 $p(t) = 100[\cos(30^\circ) + \cos(100t + 60^\circ)] = 50\sqrt{3} + 100 \cos(100t + 60^\circ)$ [W]

7.2 $P = \frac{VI}{2} \cos(\theta_V - \theta_I) = \frac{(10)(5\sqrt{2})}{2} \cos(-15^\circ + 60^\circ) = 25$ [W]

7.3 $P_{L,avg} = \frac{\mathbf{V}_L}{\sqrt{2}} \frac{\mathbf{I}_L}{\sqrt{2}} \cos(121^\circ - 31^\circ) = \frac{10.3}{\sqrt{2}} \times \frac{1.03}{\sqrt{2}} \cos(90^\circ) = 0$ [W]

7.4 $P_{avg} = \frac{1}{2}(20)(10) \cos(45^\circ - 15^\circ) = 50\sqrt{3}$ [W]

7.5 $P_{avg} = \frac{1}{2} |\mathbf{I}_S|^2 \times 5 = \frac{1}{2}(1.2649)^2 \times 5 = 5.2$ [W]

7.6 $P_{avg,max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}} = \frac{(100)^2}{8(100)} = 12.5$ [W]

7.7 $P_{avg,max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}} = \frac{(3\sqrt{10})^2}{8(10.3)} = 1.09$ [W]

7.8

(a) $V_{rms} = 5$ [V]

(b) $I_{rms} = \sqrt{(5)^2 + \frac{(3)^2}{2}} = 5.43$ [A]

(c) $V_{rms} = \sqrt{\frac{(7)^2 + (3)^2}{2}} = 5.39$ [V]

$$7.9 \quad V_{rms} = \sqrt{4} = 2 \text{ [V]}$$

$$7.10 \quad pf = \cos(18.43^\circ) = 0.949$$

$$7.11 \quad pf = \cos(-45^\circ) = 0.707$$

$$7.12 \quad \mathbf{S} = 180 - j311.77 \text{ [VA]}$$

피상 전력: $P_{app} = |\mathbf{S}| = 360 \text{ [VA]}$

평균 전력: 180 [W]

무효 전력: -311.77 [VAR]

$$7.13 \quad \mathbf{S} = 204.79 + j143.39 \text{ [VA]}$$

피상 전력: $P_{app} = |\mathbf{S}| = 250 \text{ [VA]}$

평균 전력: 204.79 [W]

무효 전력: 143.39 [VAR]

$$7.14 \quad \mathbf{S} = 1058.92 + j332.45 \text{ [VA]}$$

피상 전력: $P_{app} = |\mathbf{S}| = 1109.88 \text{ [VA]}$

평균 전력: 1058.92 [W]

무효 전력: 332.45 [VAR]

$$7.15 \quad C = \frac{Q_c}{\omega \mathbf{V}^2} = \frac{390}{(2\pi)(50)(100)^2} = 124.2 \text{ [\mu F]}$$

$$7.16 \quad C = \frac{2Q_c}{\omega \mathbf{V}_s^2} = \frac{(2)(400)}{(2\pi)(60)(100)^2} = 212.3 \text{ [\mu F]}$$

7.17

abc 위상 순서

$$\mathbf{V}_{an} = \frac{100\sqrt{3}}{\sqrt{3}\angle 30^\circ} = 100 \angle -30^\circ$$

$$\mathbf{V}_{bn} = 100 \angle (-30^\circ - 120^\circ) = 100 \angle -150^\circ$$

$$\mathbf{V}_{cn} = 100 \angle 90^\circ$$

acb 위상 순서

$$\mathbf{V}_{an} = \frac{100\sqrt{3}}{\sqrt{3}\angle -30^\circ} = 100\angle 30^\circ$$

$$\mathbf{V}_{cn} = 100\angle(30^\circ - 120^\circ) = 100\angle -90^\circ$$

$$\mathbf{V}_{bn} = 100\angle 150^\circ$$

7.18

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{300\angle 0^\circ}{10\angle -36.87^\circ} = 30\angle 36.87^\circ [\text{A}]$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 30\angle(36.87^\circ - 120^\circ) = 30\angle -83.13^\circ [\text{A}]$$

$$\mathbf{I}_c = \mathbf{I}_b \angle -120^\circ = 30\angle(-83.13^\circ - 120^\circ) = 30\angle 156.87^\circ [\text{A}]$$

$$\mathbf{V}_{ab} = \sqrt{(450)^2 + (150\sqrt{3})^2} \angle \tan^{-1}\left(\frac{\sqrt{3}}{3}\right) = 474\angle 30^\circ [\text{V}]$$

$$\mathbf{V}_{bc} = 474\angle(30^\circ - 120^\circ) = 474\angle -90^\circ [\text{V}]$$

$$\mathbf{V}_{ca} = 474\angle(-90^\circ - 120^\circ) = 474\angle +150^\circ [\text{V}]$$

7.19 $\mathbf{I}_b = 16.48\angle -104.05^\circ [\text{A}], \quad \mathbf{I}_L = |\mathbf{I}_b| = 16.48 [\text{A}]$

7.20 $\mathbf{I}_n = 2.49\angle -48.9^\circ [\text{A}]$

Chapter 08 연습문제 해답

8.1 $\mathbf{I}_s(j\omega) = 10 \angle 0^\circ [\text{A}], R = 10 [\Omega]$,

$$j\omega L = j2 \times 1 = j2 [\Omega], \frac{1}{j\omega C} = \frac{1}{j2 \times 0.2} = -j2.5 [\Omega]$$

8.2 $\frac{\mathbf{V}_o(j\omega)}{\mathbf{V}_s(j\omega)} = 0.5 - j0.5$

8.3 $\frac{\mathbf{V}_o(j\omega)}{\mathbf{V}_s(j\omega)} = 1.5 - j0.5$

$$\frac{\mathbf{V}_o(j\omega)}{\mathbf{V}_s(j\omega)} = \sqrt{(1.5)^2 + (-0.5)^2} \tan^{-1}\left(\frac{-0.5}{1.5}\right) = 1.581 \angle -18.43^\circ$$

8.4 $\frac{\mathbf{V}_o(j\omega)}{\mathbf{V}_s(j\omega)} = \frac{(2.2 - j0.4)(13 + j)}{(13 - j)(13 + j)} = \frac{29 - j3}{170}$

8.5 $\mathbf{H}_I(j\omega) = \frac{\mathbf{I}_o(j\omega)}{\mathbf{I}_s(j\omega)} = \frac{(1 + j)(4.5 - j5)}{(4.5 + j5)(4.5 - j5)} = \frac{9.5 - j0.5}{45.25}$

8.6 $L = \frac{R}{\text{BW}} = \frac{10}{20} = 0.5 [\text{H}], C = \frac{1}{100 \times L} = \frac{1}{100 \times 0.5} = 20 [\text{mF}]$

8.7 $C = \frac{1}{R \times \text{BW}} = \frac{1}{10 \times 20} = 5 [\text{mF}], L = \frac{1}{100 \times C} = \frac{1}{100 \times 5 \times 10^{-3}} = 2 [\text{H}]$

$$8.8 \quad Q = \frac{\omega_r}{\text{BW}} = \frac{5000}{125} = 40$$

$$8.9 \quad Q = \omega_r RC = (2200)(20)(4 \times 10^{-6}) = 0.18$$

$$8.10 \quad \omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3})(50 \times 10^{-6})}} = 1000 \text{ [rad/s]}$$

$$\text{BW} = \frac{1}{RC} = \frac{1}{(10 \times 10^3)(50 \times 10^{-6})} = 2 \text{ [rad/s]}$$

$$Q = \frac{\omega_r}{\text{BW}} = \frac{1000}{2} = 500$$

$$8.11 \quad |\mathbf{H}(j2)| = \frac{2}{4(\sqrt{1^2 + 2^2})^2} = 0.1$$

8.12 저역통과 필터.

$$8.13 \quad f_0 = \frac{\omega_0}{2\pi} = \frac{2 \times 10^6}{2\pi} = \frac{10^6}{\pi} \text{ [Hz]}$$

$$\text{BW} = \frac{R}{L} = \frac{200}{10 \times 10^{-3}} = 2 \times 10^4$$

$$Q = \frac{\omega_0}{\text{BW}} = \frac{2 \times 10^6}{2 \times 10^4} = 100$$

$$8.14 \quad \text{대역통과 필터}, \quad \omega_0 = \frac{1}{(1)(1)} = 1 \text{ [rad/s]}$$

$$8.15 \quad \text{고역통과 필터}, \quad f_c = \frac{R}{2\pi L} = \frac{300}{2\pi(0.2)} = 238.6 \text{ [Hz]}$$

8.16 $\omega_c = 0.2$ [rad/s]

8.17 (a) $H = 10^{0.2} = 1.5849$ (b) $H = 10^{-0.2} = 0.6310$

8.18 영점: -20, 극점: -5, (삼중근) -2

$$8.19 H_{dB} = 20 \log_{10} 2 + 20 \log_{10} \left| 1 + \frac{j\omega}{20} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{5} \right|$$

$$\phi = \tan^{-1} \left(\frac{\omega}{20} \right) - \tan^{-1} \left(\frac{\omega}{2} \right) - \tan^{-1} \left(\frac{\omega}{5} \right)$$

$$8.20 \mathbf{H}(j\omega) = \frac{10 \left[\frac{1}{10} (10 + j\omega) \right]}{\left[\frac{1}{100} (100 + j\omega) \right] \left[\frac{1}{1000} (1000 + j\omega) \right]} = \frac{10^5 (10 + j\omega)}{(100 + j\omega)(1000 + j\omega)}$$

Chapter 09 연습문제 해답

$$9.1 \quad F(s) = -\frac{e^{-st}}{s} \Big|_0^2 + \frac{1}{s} \int_0^2 e^{-st} dt + \frac{2e^{-st}}{s} \Big|_2^4 = \frac{1}{s^2} (1 - e^{-2s} + s - 3se^{-2s} + 2se^{-4s})$$

$$9.2 \quad \mathcal{L}[\cosh at] = \frac{1}{2} \mathcal{L}[e^{at} + e^{-at}] = \frac{1}{2} \left[\int_0^\infty e^{at} e^{-st} dt + \int_0^\infty e^{-at} e^{-st} dt \right]$$

$$= \frac{1}{2} \left[-\frac{e^{-(s-a)t}}{s-a} \Big|_0^\infty - \frac{e^{-(s+a)t}}{s+a} \Big|_0^\infty \right] = \frac{1}{2} \left[\frac{1}{s-a} + \frac{1}{s+a} \right] = \frac{s}{s^2 - a^2}$$

$$\mathcal{L}[\sinh bt] = \frac{1}{2} \mathcal{L}[e^{bt} - e^{-bt}] = \frac{1}{2} \left[\int_0^\infty e^{bt} e^{-st} dt - \int_0^\infty e^{-bt} e^{-st} dt \right]$$

$$= \frac{1}{2} \left[-\frac{e^{-(s-b)t}}{s-b} \Big|_0^\infty + \frac{e^{-(s+b)t}}{s+b} \Big|_0^\infty \right] = \frac{1}{2} \left[\frac{1}{s-b} - \frac{1}{s+b} \right] = \frac{b}{s^2 - b^2}$$

$$9.3 \quad f(t) = 2u(t) - 2\delta(t) - 5e^{-3t}$$

$$9.4 \quad f(t) = 2e^{-3t} - 2e^{-t} + 4te^{-t}$$

$$9.5 \quad \mathcal{L}[\cos(t-1)u(t-1)] = \frac{se^{-s}}{s^2 + 1^2}$$

$$9.6 \quad f(t) = 2\delta(t) + e^{-2t}u(t)$$

$$9.7 \quad f(t) = f_a(t) + f_b(t) + f_c(t) = 4u(t) - 2u(t-1) + 2u(t-3) - 4u(t-4)$$

$$9.8 \quad \mathbf{Z}_{in}(s) = s \parallel \left(2 + \frac{1}{s} \right) = \frac{s \left(2 + \frac{1}{s} \right)}{s + 2 + \frac{1}{s}} = \frac{s(2s+1)}{s^2 + 2s + 1} = \frac{s(2s+1)}{(s+1)^2}$$

$$9.9 \quad \mathbf{Z}_{in}(s) = \frac{1}{s} \parallel \frac{2s^2 + 5s + 2}{3 + 2s} = \frac{\frac{1}{s}(2s^2 + 5s + 2)}{\frac{1}{s} + 3 + 2s} = \frac{2s^2 + 5s + 2}{2s^2 + 3s + 1} = \frac{(2s+1)(s+2)}{(2s+1)(s+1)} = \frac{s+2}{s+1}$$

$$9.10 \quad i(t) = 2e^{-t}u(t)$$

$$9.11 \quad \mathbf{I}(s) = \frac{12/s}{\mathbf{Z}(s)} = \frac{4}{2s+1}$$

$$9.12 \quad \mathbf{V}_1(s) = \frac{6(s+3)}{(s+2)^2}$$

$$9.13 \quad \mathbf{I}_1 = \frac{|D_1|}{|D|} = \frac{4(s+1)}{s(s^2 + 5s + 2)}, \quad \mathbf{I}_2 = \frac{|D_2|}{|D|} = \frac{4}{s^2 + 5s + 2}$$

$$9.14 \quad \mathbf{I}_1 = \frac{|D_1|}{|D|} = \frac{4(s+2)}{2s^2 + 5s + 1}, \quad \mathbf{I}_2 = \frac{|D_2|}{|D|} = \frac{4}{2s^2 + 5s + 1}$$

$$9.15 \quad v_o(t) = 2e^{-2t} - 10e^{-6t}$$

$$9.16 \quad \mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_s(s)} = \frac{10s(s+1)}{2s^2 + 12s + 5} \cdot \frac{s}{2(s+1)} = \frac{5s^2}{2s^2 + 12s + 5}$$

$$9.17 \quad \mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_s(s)} = \frac{2s^3}{3s^3 + 4s^2 + 2s + 1}$$

$$9.18 \quad \mathbf{H}(s) = \frac{\mathbf{I}_o(s)}{\mathbf{I}_s(s)} = \frac{\mathbf{V}_o(s)}{\mathbf{I}_s(s)} = \frac{2s^3}{2s^3 + 3s^2 + s + 1}$$

$$9.19 \quad \mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{I}_s(s)} = \frac{2s^3}{2s^3 + 3s^2 + s + 1}$$

$$9.20 \quad \mathbf{H}(s) = \frac{\mathbf{I}_o(s)}{\mathbf{V}_s(s)} = \frac{\mathbf{V}_o(s)}{\mathbf{V}_s(s)} = \frac{2s^3}{3s^3 + 4s^2 + 2s + 1}$$